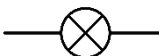


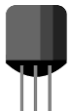

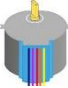


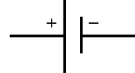

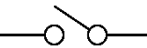

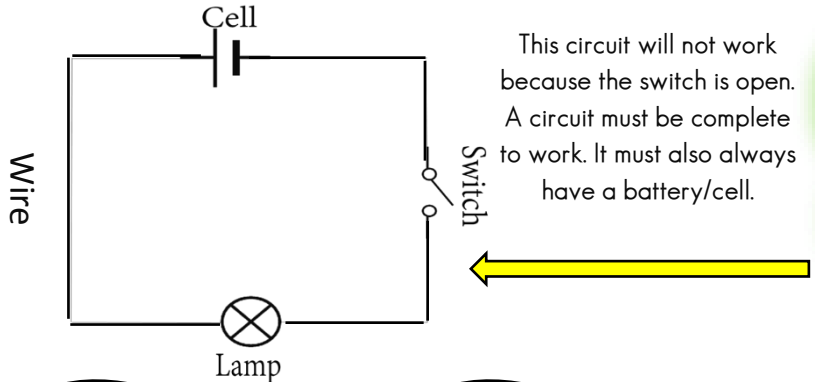



ELECTRICITY


		BULB
		BUZZER
		MOTOR
		WIRES
		BATTERY/CELL
		SWITCH



An electrical conductor lets electricity pass through. They are often metals but it also includes water.



An electrical insulator does not let electricity pass through.



DANGER! HIGH VOLTAGE!

Electricity is everywhere so always be safe. Be careful of mains switches, open sockets and any signs to do with electricity. The human body is 80% water so it conducts electricity. If someone has had a shock always turn the electricity off first, then call for help!

- 1.) If you make the wires longer, the bulb will get dimmer. This is because there is more resistance.
- 2.) If you add more bulbs, the bulbs get dimmer. This is because there is also more resistance.
- 3.) If you add more batteries, the bulbs will get brighter. This is because there is less resistance and a greater current.

